




RAMAIAH
SKILL ACADEMY

TIMING BASICS

Vasudev Murthy

Timing paths

 


Start Point:

clock pin of sequential device

End Point:

data input pin of sequential devices

 


Start Point:

clock pin of sequential device

End Point:

primary output port

 


Start Point:

primary input port

End Point:

data input pin of sequential devices

 


Start Point:

primary input port

End Point:

primary output port


Timing paths

 

- This circuit has
- How many start points ?
- How many end points ?
- How many paths ?

Timing Terminologies

 - Setup Time : Time for which data should be stable at the input of the ff **before** the arrival of clock at the ff's clock pin
- Hold Time : Time for which data should be stable at the input of the ff **after** the arrival of clock at the ff's clock pin




Timing Terminologies

- Critical Path : Theoretically path which has maximum delay
- Arrival Time : Time taken by data to reach a particular end point from a specific start point. Depends on complexity of logic through which data traverses
- Required Time : Time at which data is required at a particular end point. Depends on the requirements / specifications
- Slack : Difference in required time and arrival time. For a design to work the slack value should always be positive


Clock Skew

 - Clock feeds multimillion flip-flops
- Theoretically clock should arrive at same instance at all flip-flops – Practically impossible
- Frequency of clock may vary from cycle to cycle
- Variation in arrival of clock at clock pin of subsequent / consecutive flip-flops is known as skew



Clock Skew

 - The difference in arrival of clock at different flip-flops could be due to
 - Jitter – cycle to cycle variation in clock period due to aging of oscillator, anomalies in the pll etc
 - Clock network delay – Uncertainty in arrival of clock due to clock network and clock network component delays




Clock Skew

- Skew can be considered to be of two types
 - When clock arrives earlier than expected – generally known as negative skew
 - When clock arrives later than expected – generally known as positive skew
- +ve skew can occur when data & clock travel in same direction
- -ve skew can occur when data & clock travel in opposite directions

Frequency Calculation


- Arrival Time = $T_{\text{COMBO, Max}}$
- Required Time = $T_{\text{CP}} + T_{\text{Clock_Insertion_Delay}} - T_{\text{SETUP}}$

 - Since there is only one clock here instead of skew the possible delay on the clock line is denoted as insertion delay





- Arrival Time : $T_{\text{CLK-Q}} + T_{\text{Combo, MAX}}$

 - Required Time = $T_{\text{CP}} + T_{\text{Clock_Skew}} - T_{\text{SETUP}}$
 - Due to presence of 2 clocks the possible difference in arrival of clock is denoted as skew




Frequency Calculation

  - Arrival Time : $T_{\text{Combo, MAX}}$
- Required Time : Explicit Timing Constraint
(If Specified)
- Arrival Time = $T_{\text{clk-Q}} + T_{\text{Combo, MAX}}$
- Required Time = Typically Unconstrained Path
(Has no requirement set)




Max Frequency Calculation

 - Find The maximum Frequency for the circuit shown in figure below



Max Frequency Calculation

 - Find The maximum Frequency for the circuit shown in figure below



| | t_p | t_{su} |
|---------------|-------|----------|
| D Flip-Flop: | 20 ns | 5 ns |
| JK Flip-Flop: | 25 ns | 10 ns |
| AND Gate: | 12 ns | |
| OR Gate: | 10 ns | |

Max Frequency Calculation

- Find the maximum Frequency for the circuit shown in figure below

